

MARK SCHEME

GCSE


PHYSICS

AQA - COMBINED SCIENCE

P2 - TEST 1
ELECTRICITY
Beginner

Mark schemes

1. (a) **three** lines drawn correctly

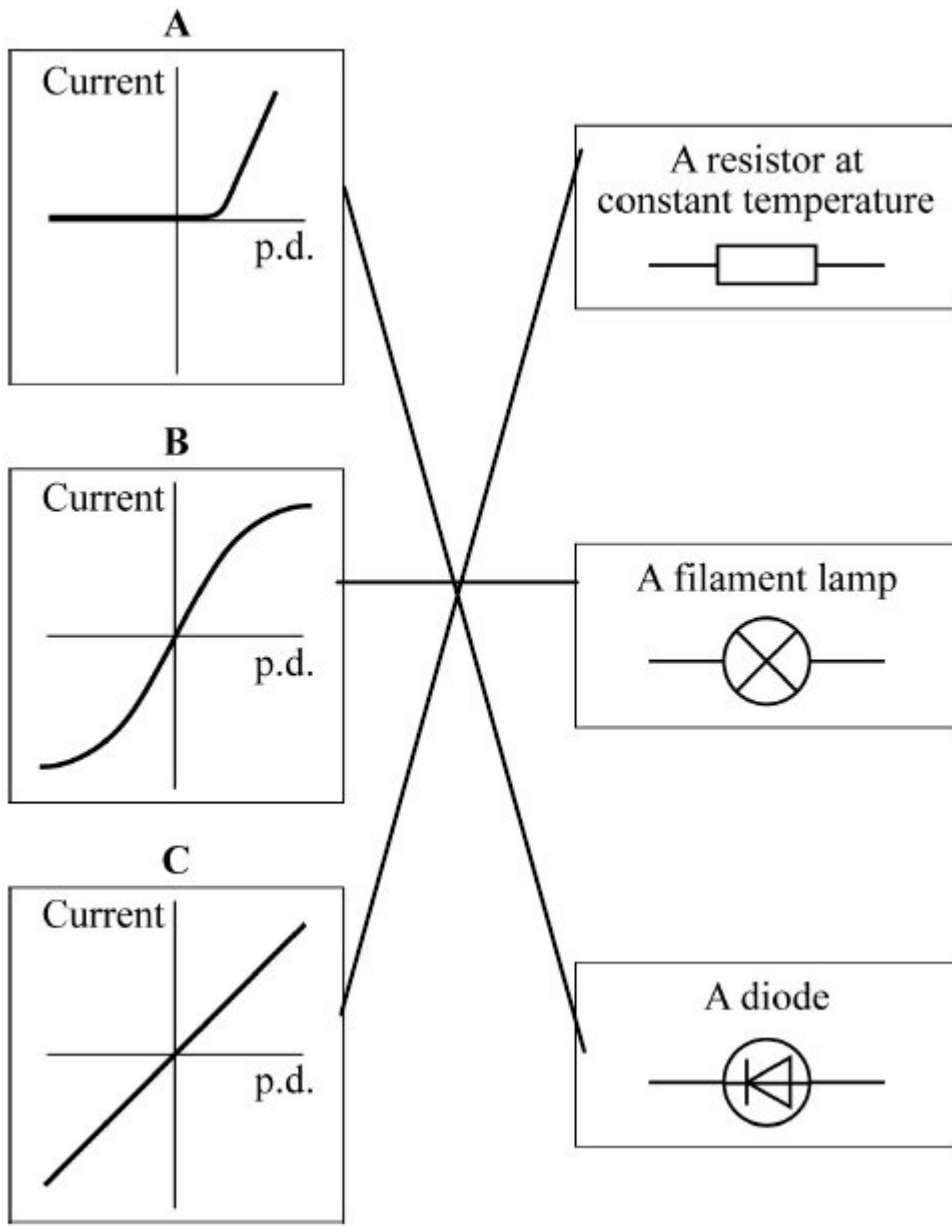

*allow 1 mark for 1 correct line
if more than one line goes from a graph, both are incorrect*

(b) **J**

2

1

[3]

2. (a) switch

allow answer circled in box

1

(b) 24

1

- (c) equal to 0.25 A 1
- (d) 4 1

[4]

3.

- (a) (i) diode
[Do not accept 'rectifier' or LED]
- (ii) lamp / bulb / light
each for 1 mark 2

- (b) • P = voltage / potential difference / p.d. / volts / V
[Allow 'Voltmeter]
- Q = current / amperes / amps / A
[Allow 'ammeter]
each for 1 mark 2

[4]

4.


- (a) ammeter anywhere in series in the circuit
accept just letter A or box with A
- voltmeter across **or** in parallel with the fixed resistor only
accept just letter V or box with V 2

- (b) (i) four correct plots
deduct one for any incorrect plot
- a straight line through the points
no requirement to extrapolate through origin
*do not credit bar charts unless correct line drawn **or** correct points* 2


- (ii) 0.25
ecf rule applies if graph is wrongly plotted 1

[5]

5. (a) circuit symbol for a lamp correct

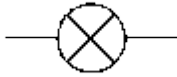

accept

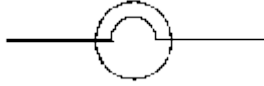

accept any standard of drawing providing circuit would work



1

circuit symbol for a cell correct

1

2 lamps drawn in parallel with 3 cells

polarity of cells must be correct (+ to -) but cells may be either way around

1

(b) 4.5

1


(c) the same as

accept any clear indication of the correct answer

1

[5]

6. (a) all 3 lines drawn correctly

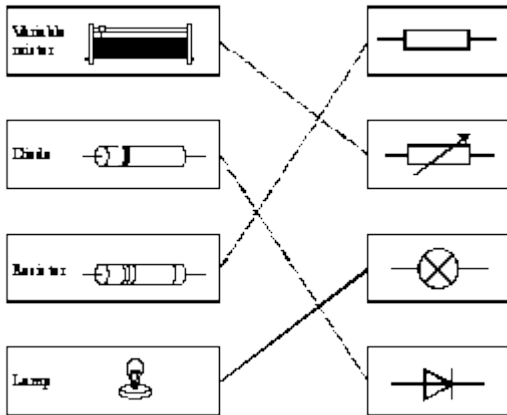

(1 only correct, 1 mark)

deduct one mark if more than one line from or to a single box

2

(b) (i) series

1

(ii) any **one** from:

- both lamps **or** lights must be on together
- if one blows, the other goes out
- switch controls both bulbs
*do **not** accept bulbs dimmer*

1

(iii) any **two** from

- each lamp **or** light can be switched on independently
- if one lamp blows the other stays on
- switching the second lamp on does not affect brightness of first
or bulbs brighter (than in first circuit) or energy explanation

2

[6]

7.

(a) **A**

1

(b) **C**

1

(c) **C**

1

(d) **B**

1

(e) a series circuit has only one path/loop/branch

1

a parallel circuit has a branch(es) to provide more than one path / loop

allow answers that describe the difference in terms of potential difference, current or resistance

1

(f) **R**

1

(g) **P**

1

(h) $Q = 0.97 \times 60$

1

$Q = 58.2$ (C)

1

$Q = 58$ (C)

an answer of 58 (C) scores 3 marks

1

[11]

8.

(a) 230 V

1

(b) Earth

must be in the correct order

1

Neutral

1

(c) It is easy to identify each wire.

1

(d) current

must be in the correct order

1

shock

1

(e) 50 Hz

1

(f) output = 25×16

1

400 (kV)

1

allow 400 (kV) with no working shown for 2 marks

(g) It reduces the energy lost due to heating

1


(h) It is safer for consumers

1

[11]

9.

(a)

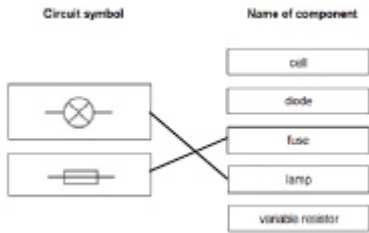

extra lines from circuit symbols negate the mark

1
1

(b) charge

1

(c) 0.13 (A)

1

(d) 0.56×300

1

168 (C)

an answer of 168 (C) scores 2 marks

1

(e) 168×4.5

1

756 (J)

an answer of 756 (J) scores 2 marks

allow ecf from part (d)

1

(f) decreases to zero

allow reads zero

1

(g) (A1) decreases to zero

allow reads zero

1

(A2) decreases

do not accept 'to zero' for A2

1

(h) thermistor

1

(i) answer in range 160–165 (Ω)

1

[13]

10.

(a) 2100 W

1

(b) power = potential difference \times current

1


(c) 50 (Hz)

1

(d) direct current (dc) only

1

(e)

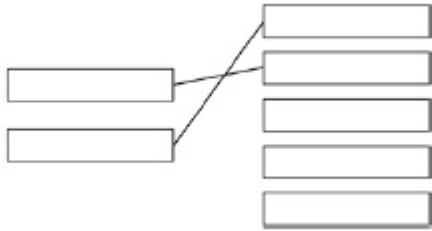

1

1

(f) green **and** yellow

both colours required

1

(g) any **two** from:

- good conductor
- hard
- corrosion resistant

2

(h)

Level 2: Scientifically relevant facts, events or processes are identified and given in detail to form an accurate account.	3-4
Level 1: Facts, events or processes are identified and simply stated but their relevance is not clear.	1-2
No relevant content	0
Indicative content allow voltage / volts / pd for potential difference <ul style="list-style-type: none">• cables transmit electricity at very high potential differences• transformers change the potential difference• step up transformer increases potential difference• overhead cables transfer electricity at a higher potential difference• step down transformer decreases potential difference• the potential difference to the consumers is much lower than the potential difference from the power station• the potential difference to the consumers is much lower than the potential difference in the cables	

4
[13]