

MARK SCHEME

GCSE

PHYSICS

AQA - TRIPLE SCIENCE

P2 - TEST 6
ELECTRICITY
Advanced

Mark schemes

1.

(a) 125

allow 1 mark for obtaining time period = 0.008 (s)

or

frequency = 1 / time period (or their calculated time period)

2

hertz

or

Hz

do not accept hz

1

(b) 50 (hertz)

1

[4]

2.

(a) potential difference

allow p.d.

allow voltage

1

temperature

1

in this order only

(b) the current increases (when the potential difference increases)

1

(which) causes the temperature of the filament to increase

1

(so) the resistance increases

do not accept resistance increases and then levels off

1

(c) a higher proportion / percentage of the (total) power / energy input is usefully transferred

wastes less energy is insufficient

or

higher (useful) power / energy output for the same (total) power / energy input

1

(d) potential difference increases

1

current decreases

1

(e) 1000 (Ω)

reason only scores if $R = 1000 (\Omega)$

1

potential difference is shared in proportion to the resistance

allow a justification using a correct calculation

1

(f) $12 = I \times 7000$

1

$$I = \frac{12}{7000}$$

1

$$I = 1.71 \times 10^{-3} \text{ (A)}$$

an answer that rounds to 1.7×10^{-3} (A) scores 3 marks

1

$$I = 1.7 \times 10^{-3} \text{ (A)}$$

this answer only

or

$$I = 0.0017 \text{ (A)}$$

an answer of 2.4×10^{-3} (A) scores 2 marks

*if no other marks scored allow 1 mark for calculation of total resistance
(7000 Ω)*

1

an answer of 1.7×10^{-3} (A) scores 4 marks

[14]

3.

(a) current

1

(b) $4.2 = 3.5 \times 10^{-3} \times R$

1

$$R = 4.2 / 3.5 \times 10^{-3}$$

1

$$R = 1200 \text{ (Ω)}$$

an answer of 1200 (Ω) scores 3 marks

an answer of 1.2 scores 2 marks

1

(c) conversion from minutes to seconds (300 s)

1

$$Q = 0.0035 \times (5 \times 60)$$

1

$$Q = 1.05 \text{ C}$$

an answer of 1.05 (C) scores 3 marks

an answer of 17.5 scores 1 mark

an answer of 1050 or 0.0175 scores 2 marks

1


(d) (potential difference) increases

1

(because thermistor) resistance increases

2nd mark dependent on scoring 1st mark

1

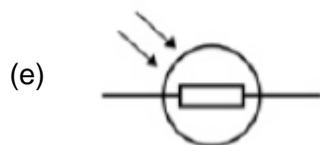


1

[10]

4.

(a)

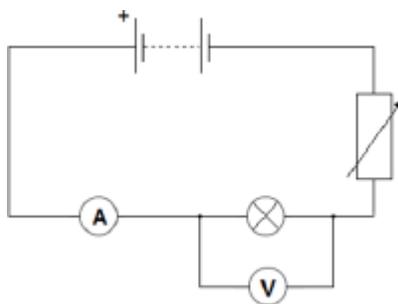

battery in series with bulb and ammeter

1

voltmeter in parallel with bulb

1

variable resistor

or

variable power pack

or

potentiometer

1

(b) A is brighter because it has a higher current (than lamp B at any p.d.)

1

(therefore A has a) higher power output (than bulb B)

accept higher energy output per second

1

- (c) lower current (than lamp A) for the same potential difference

accept answer in terms of $R = V / I$

allow reference to a comparison of the gradients

1

this is true for all values (of p.d. on the graph)

1

- (d) 0 – 2 Volts

allow a range from 0 V up to any value between 1 and 2 V.

1

(for an ohmic conductor) current is directly proportional to potential difference

allow lines (of best fit) are straight and pass through the origin

1

(so) resistance is constant

1

[10]

5.

- (a) current at 0.5 V = 0.91 (A)

1

$$P = 0.91 \times 0.5$$

1

$$P = 0.455 \text{ (W)}$$

an answer of 0.455 (W) scores 3 marks

1

- (b) straight line with positive gradient

allow for 1 mark a straight line that passes through (0.1, 0)

1

positive y-axis intercept

ignore any values on y-axis

1

- (c) $0.15 = \frac{0.52}{\text{total P}}$

1

$$\text{total P} = 3.47 \text{ (W)}$$

1

$$\text{area} = \frac{3.47}{450}$$

1

$$\text{area} = 7.7 \times 10^{-3} \text{ (m}^2\text{)}$$

an answer of $7.7 \times 10^{-3} \text{ (m}^2\text{)}$ scores 4 marks

allow use of student's calculated incorrect total power for last 2 marking points

1

(d) connect the solar cells in parallel

1

(so that) the current has multiple paths it can take

or

the total resistance is less than the resistance of one solar cell

1

[11]

6.

(a) (i) 1.7

1

(ii) 51

or

30 × their (i) correctly calculated

allow 1 mark for correct substitution i.e. $1.7 = \frac{Q}{30}$

or their (i) = $\frac{Q}{30}$

2

coulomb / C

do not accept c

1

(iii) 612

or

their (ii) × 12 correctly calculated

or

their (i) × 360 correctly calculated

allow 1 mark for correct substitution i.e. $E = 12 \times 51$

or $12 \times$ their (ii)

or their (i) × 360

2

- (b) ions vibrate faster
or
 ions vibrate with a bigger amplitude
accept atoms for ions throughout
accept ions gain energy
accept ions vibrate more
ions start to vibrate is insufficient

1

electrons collide more (frequently) with the ions

or

(drift) velocity of electrons decreases

electrons start to collide is insufficient

there are more collisions is insufficient, unless both electrons and ions are implied

1

[8]

7.

- (a) (i) 2

allow 1 mark for correct substitution i.e. 0.8×2.5 provided no further step shown

2

- (ii) straight line drawn from origin to 2, 0.8

or

their (a)(i), 0.8

1

curve from 2, 0.8 to 12,2

or

their (a)(i) 0.8 to 12,2

accept curve from 2, 0.9 to 12,2

or

their (a)(i) 0.9 to 12,2

'convex' curve required

accept a curve that flattens between 10 and 12V

1

- (iii) filament / lamp gets hot

accept temperature increases

1

- (b) 108


allow 1 mark for correct substitution i.e. 1.5×72 provided no further step shown

2

[7]

8.

(a) (i)

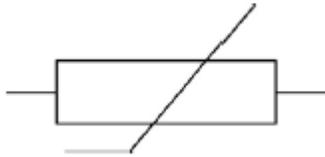


1

(ii) 360

allow 1 mark for correct substitution, ie $9 = 0.025 \times R$

2

(iii) sketch graph of correct shape, ie

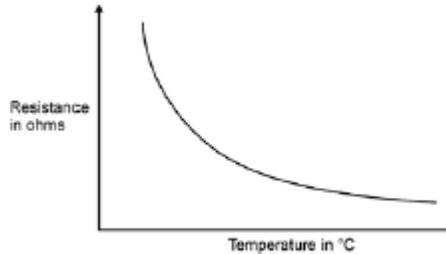

1

(iv) An automatic circuit to switch a heating system on and off.

1

(b) so ammeter reduces / affects current as little as possible

accept so does not reduce / change the current (it is measuring)

accurate reading is insufficient

not change the resistance is insufficient

1

(c) gives a common understanding

accept is easier to share results

accept can compare results

do not need to be converted is insufficient

prevent errors is insufficient

1

(d) replace Bunsen (and water) with a lamp

accept any way of changing light level

1

replace thermometer with light sensor

accept any way of measuring a change in light level

datalogger alone is insufficient

1

[9]

9.

(a) diode

accept LED

1

- (b) all symbols correct
must include at least voltmeter and diode

1



allow ecf from part (a) if the component is not identified as a diode
allow symbol without the line through triangle
ignore polarity of diode

voltmeter in parallel with component added in series
any additional components must not affect the ability to measure V and I for the diode / their (a)

1

- (c) (i) 0.05
accept 50 mA
accept between 0.048 and 0.050 inclusive

1

- (ii) 16

$$\frac{0.8}{0.05}$$
their (c)(i) correctly calculated gains both marks
allow 1 mark for correct transformation and substitution

$$\frac{0.8}{0.05} \text{ or } \frac{0.8}{\text{their (c)(i)}}$$
allow 17 if using 0.048

2

[6]

- 10.** (a) (i) 50(Hz)
ignore any unit given

1

- (ii) any **two** from:
- (some) current flows to Earth
accept ground for Earth
 - current flows through copper braid
accept current flows through the earth wire
accept electricity for current in either the first or second marking point but not both
 - RCCB detects difference between current in live and neutral wire

2

(iii) can be reset
accept does not need replacing

or

faster acting
accept switches circuit off faster

1

(b) (i) 79 200

allow 1 mark for correct substitution, ie $11 = \frac{Q}{2 \times 3600}$

an answer 22 gains 1 mark

2

coulombs / C

*do **not** accept c*

1

(ii) 18 216 000

*accept for 2 marks 18 216 kJ **or** 18.216 MJ*

or

230 × their (b)(i) correctly calculated

*allow 1 mark for correct substitution, ie 230 × their (b)(i) **or***

allow 1 mark for power calculated as 2530(W)

2

(c) increases temperature of thermistor

1

changes resistance (of thermistor)

*do **not** accept increases resistance (of thermistor)*

an answer decreases resistance (of thermistor) gains 2 marks

1

[11]